

---

# Analog Design

- Electronic Design Automation Tools and Foundry Access
- Analog CMOS Circuit Design
- Packaging, Interconnect and Systems Issues

Paul O'Connor, Brookhaven National Laboratory


IEEE Nuclear Sciences Symposium/Medical Imaging Conference

October 24, 2009
 
# Electronic Design Automation (EDA)

---

- Commercial: Cadence, Mentor, Synopsys, Tanner
- Public domain: <http://www-cad.eecs.berkeley.edu/software.html> is a good starting point. See also <http://bach.ece.jhu.edu/~tim/programs/magic/> for Magic, a VLSI Layout Editor.




# Essential tools for circuit-level design


---

- Transistor-level circuit simulator
  - *Matrix solution of network equations of your circuit*
  - *PSPICE, HSPICE, SPECTRE are the standards*
  - *inputs: circuit topology, device models, source driving functions*
  - *Outputs:*
  - *DC bias point, source sweep, temperature sweep*
  - *Frequency sweep using linearized model of active devices*
  - *Noise analysis in freq. domain*
  - *Time sweep*
  - *Monte-Carlo facility, samples from user-defined parameter distributions*
- Transistor models
  - *Strike a balance between*
    - Accurate in all transistor operating regions
    - Physics-based
      - Surface-potential based
      - Inversion charge based
    - Computational efficiency
    - Simple parameter extraction methodology
  - *Recent interest in high frequency CMOS design for RF applications has led to improved analog models*
  - *BSIM, EKV, MOS9 for advanced CMOS*
  - *Usually supplied by foundry*


# SPICE input & outputs

 

 
Schematic entry with backannotated node voltages and currents



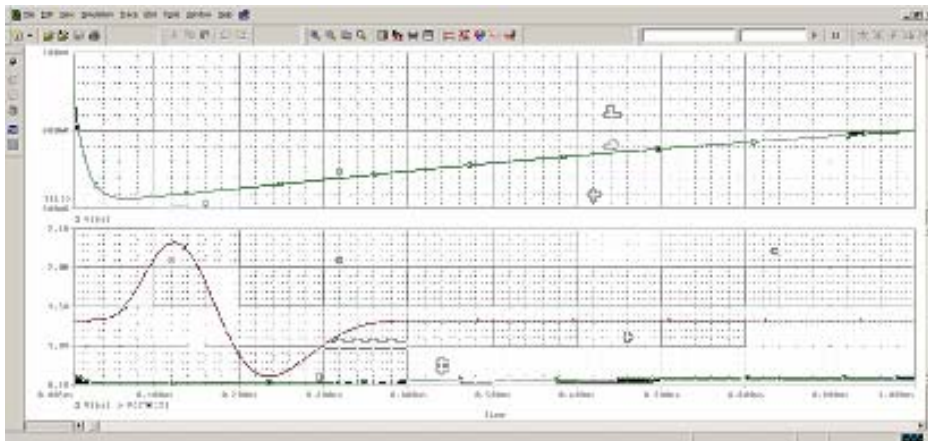Noise analysis: equivalent input noise density vs. frequency



 Transient analysis result: voltages vs. time



Monte Carlo analysis: node voltage vs. temperature, 50 runs from parameter distribution




# EDA tools for physical design

---

- Chip layout (full custom, no pre-designed blocks)
  - *Polygon-level mask editor with built-in process knowledge*
- Design rule checker
  - *Checks mask geometry, flags violations of foundry design rules*
- Connectivity verification
  - *Layout-to-schematic network comparison*
- Parasitic extraction
  - *Find capacitance, resistance associated with interconnect lines on chip*

# Layout with MAGIC

 


Analog and digital layout, 1.2μm CMOS


\*\*\*\*\* top level cell is ./preampflat.ext

```
C1 IN 2 5.00932e-13
Cxxnull 2 vss 1.323e-13
M1 BGND IN 1 GND! nch M=48 W=87.6U L=1.2U GEO=3
M2 1 VB1 Vdd Vdd pch M=2 W=42.0U L=3.0U GEO=3
M3 3 VB1 Vdd Vdd pch W=30.0U L=3.0U GEO=3
M4 VSS 2 3 Vdd pch W=12.0U L=1.8U GEO=3
M5 2 BGND 1 Vdd pch M=6 W=83.4U L=1.2U GEO=3
M6 2 VB2 VSS GND! nch W=199.8U L=40.2U GEO=3
M7 VSS VB2 OUT GND! nch M=3 W=199.8U L=40.2U GEO=3
M8 OUT 3 Vdd GND! nch M=24 W=87.6U L=1.2U GEO=3
R1 IN 3 57166.5
C3 9_2072_18# OUT 1.0F
C4 9_226_18# BGND 1.0F
C5 1 VSS 2.3F
C6 BGND IN 8.6F
C7 Vdd 3 3.0F
C8 9_720_18# BGND 1.0F
C9 1 IN 5.3F
C10 BGND Vdd 1.8F
C11 OUT 3 4.2F
C12 Vdd VSS 1.1F
C13 OUT VB2 3.8F
C14 VSS VB2 6.2F
C15 9_1806_18# OUT 1.0F
C16 OUT VSS 2.6F
C17 BGND VSS 4.3F
C18 Vdd VB1 1.1F
C19 1 GND 404.4F
C20 2 GND 79.6F
C21 3 GND 98.5F
C22 9_2072_18# GND 1.0F
C23 VSS GND 439.1F
C24 Vdd GND 447.6F
C25 BGND GND 449.7F
C26 9_226_18# GND 1.0F
C27 9_720_18# GND 1.0F
C28 OUT GND 275.9F
C29 IN GND 149.9F
C30 9_1806_18# GND 1.0F
C31 VB1 GND 23.2F
C32 VB2 GND 96.3F
.END
```

 Circuit netlist extracted from layout w/  
parasitic capacitances




← 6 mm →

 

Mixed-signal circuit,  $6 \times 10^5$  transistors, 0.25μm CMOS

# Graphical Design Rule Check

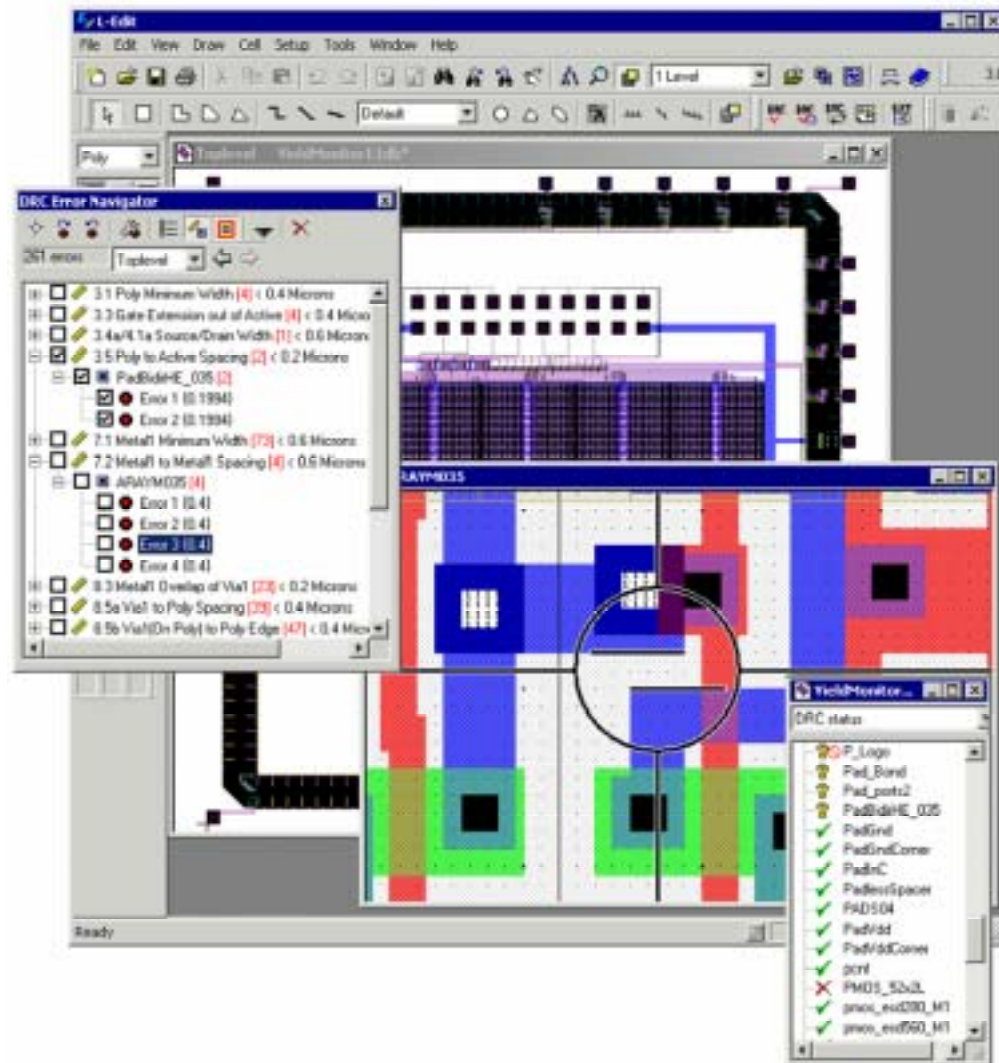

# Multiproject services for low-cost prototyping

- Organize regularly-scheduled multiproject runs (MPW)
- Collect and merge designs and provide production-compatible masks to foundry
  - *share costs among users*
    - mask-area weighted
- Access to latest production processes from major foundries
  - *CMOS, BiCMOS, SiGe, (GaAs, InP, MEMS)*
- User support:
  - *design kit*
  - *models*
  - *parametric process data*
    - process control monitor and reference design probed after each MPW run
    - statistical process database
    - quality/yield monitor
  - *access to wafer thinning, dicing, wirebonding, and packaging services*
  - *low-volume production*

# Multiproject services

---

- Multi-foundry:

- *MOSIS*

[www.mosis.org](http://www.mosis.org)

- *Europractice*

[www.imec.be/europractice](http://www.imec.be/europractice)

- *Canadian Microelectronics Corp.*

[www.cmc.ca](http://www.cmc.ca)



- Foundry-based:

- *TSMC*

[www.tsmc.com](http://www.tsmc.com)

- *XFAB*

[www.xfab.com](http://www.xfab.com)

- *Zfoundry*

[www.zfoundry.com](http://www.zfoundry.com)


- *Jazz Semicond.*

[www.jazzsemi.com](http://www.jazzsemi.com)




# MPW examples

wafer

 

reticle (0.18 $\mu$ m CMOS)

 

Cost comparison


Process	chip size	lot size	cost
	mm <sup>2</sup>	no. parts	\$K
1.5 $\mu$ m CMOS	5	5	1.1
0.5 $\mu$ m CMOS	5	40	6.5
0.35 $\mu$ m CMOS	15	40	20.7
0.25 $\mu$ m CMOS mixed	25	40	47.3
0.18 $\mu$ m CMOS	50	40	126.8
0.35 $\mu$ m SiGe BiCMOS	50	40	90.0

[www.mosis.org](http://www.mosis.org)

# Engineering run costs

---


Typical engineering  
run = 20 wafers

 

# Technology introduction roadmap

## MOSIS and Semiconductor Industry Association

---

 



---

# Analog CMOS Circuit Design


Paul O'Connor, Brookhaven National Laboratory

IEEE Nuclear Sciences Symposium/Medical Imaging Conference

October 24, 2009


# Signal Chain Block Diagram

---

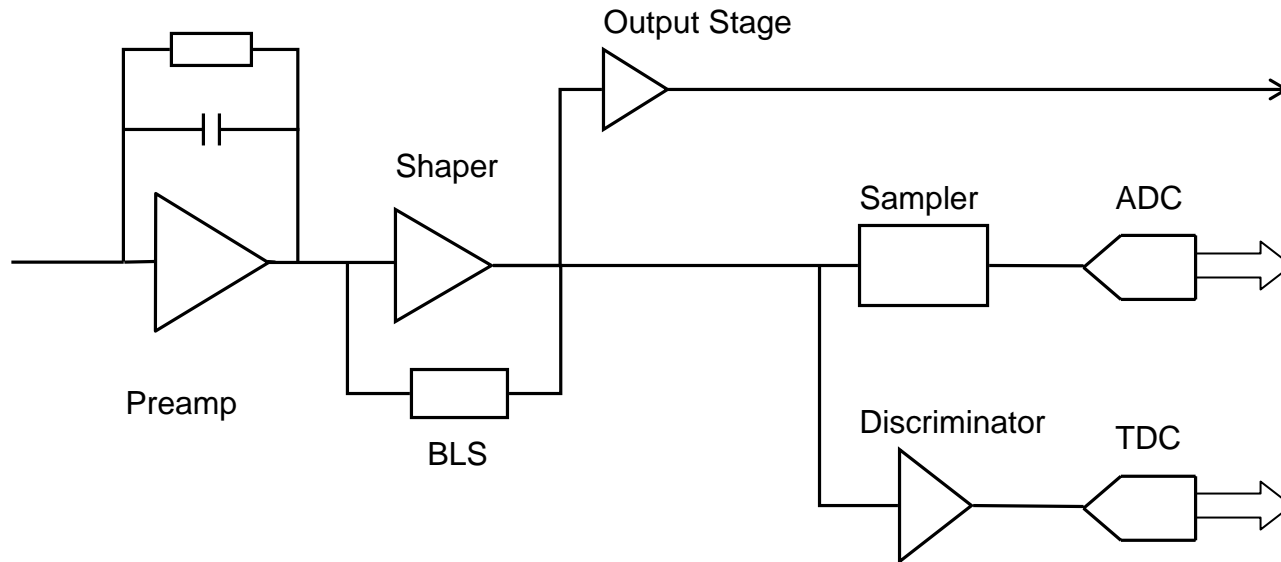


# Charge Sensitive Preamplifier

---

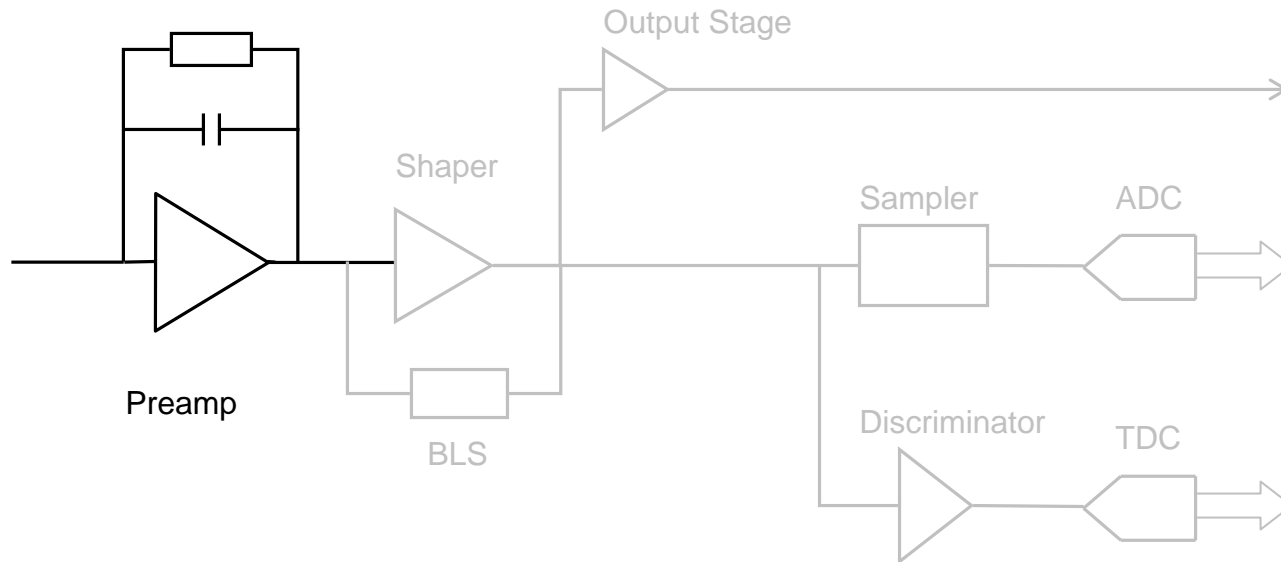
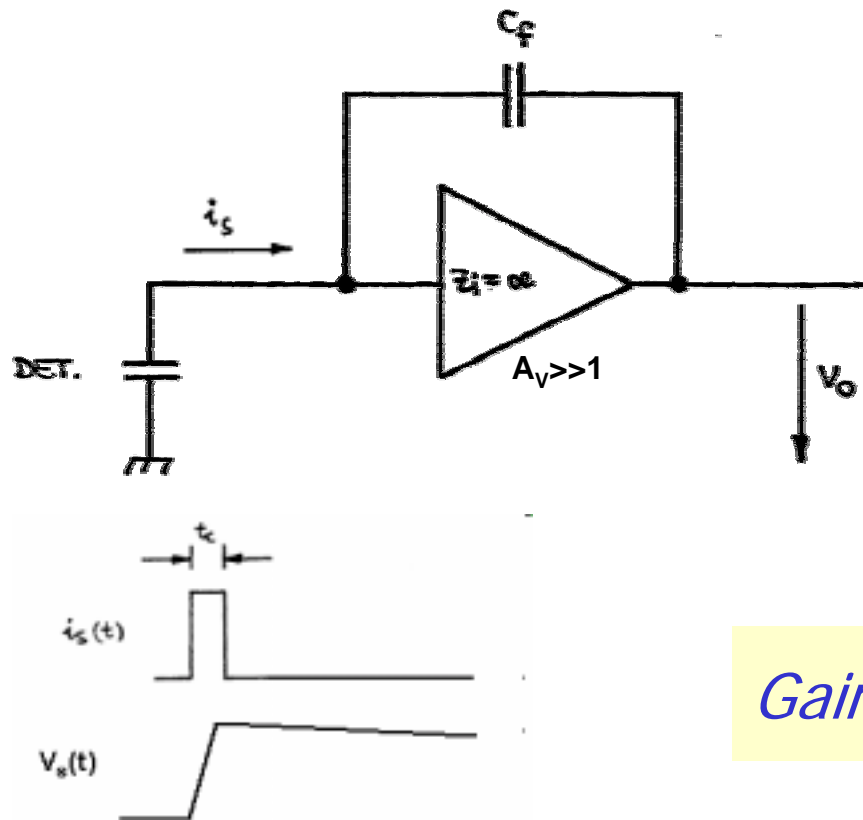
# Low noise charge amplification

- Charge sensitive configuration (active integrator)



for  $Z_{in}, |A_v| \rightarrow \infty$

$$V_s = \frac{\int i_s(t) dt}{C_f} = \frac{Q_s}{C_f}$$

*Gain insensitive to  $C_{det}$  and  $A_v$*


# MOS charge amplifier design

- Key parameters:


- $C_{det}$ ,  $I_{det}$ ,  $Q_{max}$  (detector)
- $Rate$ ,  $P_{diss}$  (system)
- $f_T$ ,  $K_F$ ,  $I_{in}$  (technology)

- Key design decisions

 
- *NMOS/PMOS*
- $L_g$
- $C_{gs}/C_{det}$
- *Reset system*
- *Weighting function*



# Charge amplifier noise sources

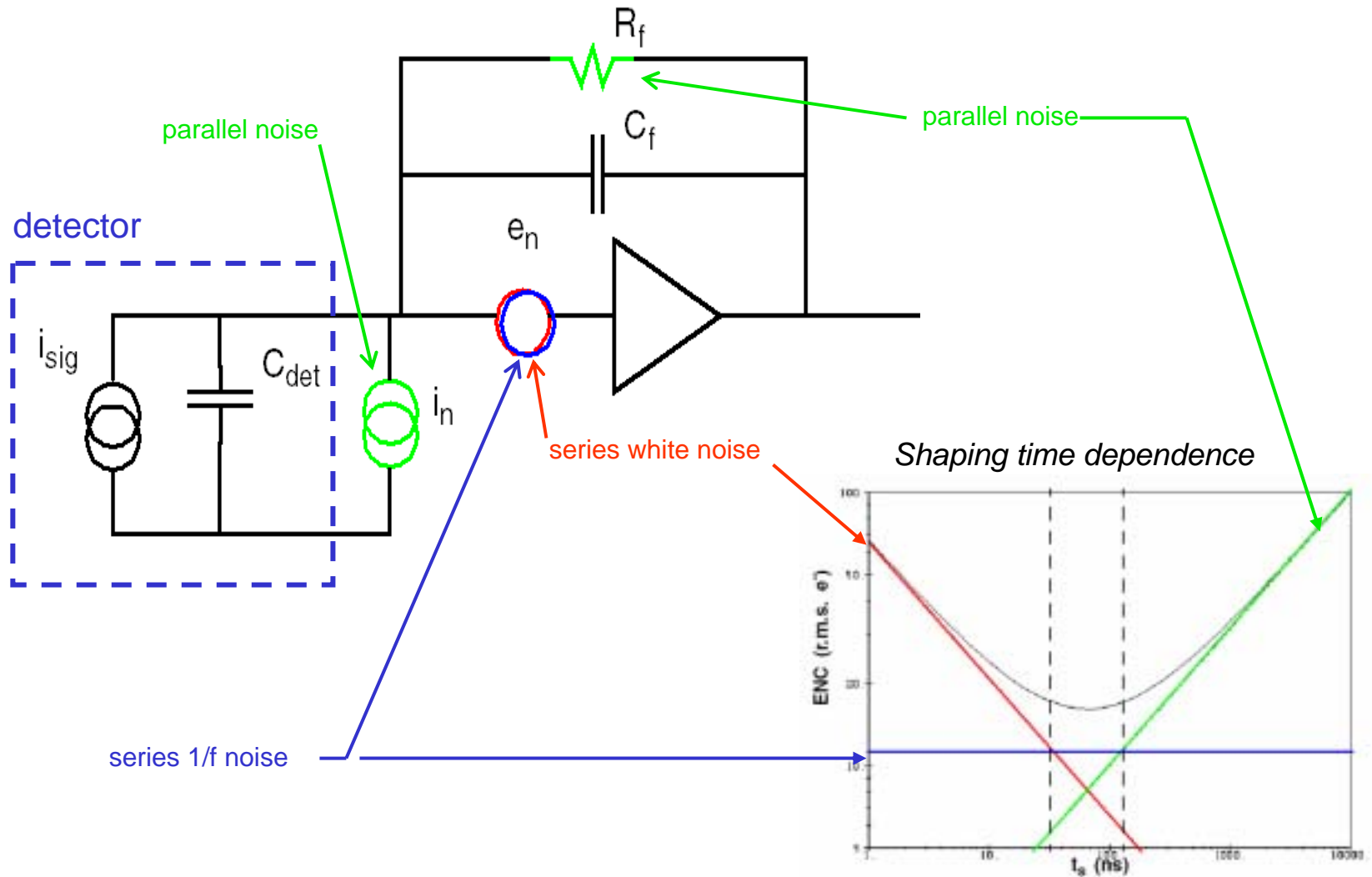
 
# Dimensioning the input MOSFET for minimum noise



Choose minimum L for best  $g_m/C_{gs}$  ratio

Increasing M1 width makes  $e_n$  smaller while  $C_{gs}$  gets larger

⇒ **optimum width for M1 must exist**

1/f noise:

$$C_{gs,opt} = C_{det}$$

White -- two cases :

I. Fixed  $V_{gs}$  (fixed current density, fixed  $f_T$ )

$$g_m \propto C_{gs}$$

$$C_{gs,opt} = C_{det}$$

II. Fixed  $I_D$  (practical case)


$$g_m \propto C_{gs}^{1/2} \text{ [strong inversion]}$$

$$C_{gs,opt} = C_{det}/3$$

$$ENC^2 = (C_{det} + C_{gs})^2 \cdot \left( \underbrace{\frac{4kT\gamma}{g_m t_m}}_{\text{white}} + \underbrace{\frac{K_F}{C_{gs}}}_{1/f} \right)$$
 
# Composite noise

- $C_{det} = 3 \text{ pF}$
- $t_p = 0.5 \text{ } \mu\text{s}$
- $P_{diss} = 1 \text{ mW}$
- $I_{leak} = 100 \text{ pA}$
- Technology:  $0.35 \text{ } \mu\text{m}$  NMOS
- *Optimum width for series noise is a compromise between white and 1/f components*





# Optimizing the input MOSFET using advanced models

Series noise “**capacitive match**” problem:

$$ENC^2 = ENC_{sw}^2 + ENC_f^2$$

$$ENC_{sw}^2 = \frac{a_1}{2\tau_p} e_{n,sw}^2 (C_d + C_{in})^2$$

$$e_{n,sw}^2 = \frac{4kTn\gamma}{g_m}$$

$$ENC_f^2 = a_2\pi \frac{K_F}{C_{ox}WL} (C_d + C_{in})^2$$

$\gamma$  and  $g_m$  depend on region of operation:

	$\gamma$	$g_m$
weak	1/2	$qI_D / nkT$
strong	2/3	$\sqrt{2\mu C_{ox} \frac{W}{L} I_D}$

*How to handle moderate inversion?*

- G.De Geronimo, P.O'Connor, V. Radeka and B. Yu, “Front-end electronics for imaging detectors”, *Nuclear Instrum. Methods* A471 (2001) 192-199
- P. O'Connor and G.De Geronimo, “Prospects for charge sensitive amplifiers in scaled CMOS”, *Nuclear Instrum. Methods* A484 (2002) 713-725
- L. Fabris, P. Manfredi, “Optimization of front-end design in imaging and spectrometry applications with room temperature semiconductor detectors”, *IEEE Trans Nucl. Sci.*, 49 (4) ,1978 –1985, Aug. 2002
- M. Manghisoni, L. Ratti, V. Re, and V. Speziali, “Submicron CMOS Technologies for Low-Noise Analog Front-End Circuits”, *IEEE Trans. Nucl. Sci.* 49,1783-1790, Aug. 2002

# Simplified EKV model for hand calculations

- substrate-referenced compact MOS model
- small, physics-based parameter set
- continuous modeling of weak to strong inversion
- simple set of equations valid for saturation:

Inversion coefficient  $i = I_D / I_0$

$$I_0 = 2n\beta \cdot U_T^2 \quad \beta = \mu \cdot C_{ox} \frac{W}{L} \quad U_T = \frac{kT}{q}$$

Interpolation function :

$$f(i) = \frac{1}{2} \left( \sqrt{1 + 4i} + 1 \right)$$

short-channel effects not modeled




$$\frac{g_m}{I_D} = \frac{1}{n \cdot U_T} \frac{1}{f(i)}$$


$$\frac{C_{GS}}{WLC_{ox}} = \frac{1}{\frac{3}{2} + \frac{f(i)}{i}}$$

$$\frac{S_{th}}{4kTng_m} = \frac{\frac{1}{2} + \frac{2}{3}i}{1+i} \equiv \gamma$$

# $g_m$ vs. $C_G$ vs. scaling

 

 
# White series noise vs. $C_G/C_d$ vs. scaling



# White series ENC, $C_{G,opt}/C_{DET}$ vs. $C_{DET}$


## NMOS

 

For fixed power budget,

$$ENC \propto \begin{cases} C_{DET}, & \text{weak inversion} \\ C_{DET}^{3/4}, & \text{strong inversion} \end{cases}$$

## PMOS

 


Power allowed to scale with  $C_{DET}$ :

$$ENC \propto C_{DET}^{1/2}$$
 
# Optimized noise vs. power

(MOSFET optimized at each power level and shaping time)





Note:

$$\left| \frac{dN}{dP} \right| \leq 0.4$$

Cd = 1pF  
0.25 μm CMOS
  
# 0.25 $\mu\text{m}$ CMOS optimized noise/power






Enhanced noise model incorporates:

- Gate capacitance bias dependence
- Gate-source and gate-drain overlap capacitance
- Length-dependent  $1/f$  noise coefficient
- $1/f^\alpha$  behavior of low-frequency noise
   
# Choice of PMOS vs. NMOS

- *PMOS lower 1/f noise*
- *NMOS white series noise advantage over PMOS diminishes each generation*
- *PMOS can be operated at reverse  $V_{BS}$  to reduce bulk resistance noise*
- *PMOS lower tunneling current at ultra-thin  $t_{ox}$*
- *Single-supply operation of PMOS-input preamp awkward:*





# Minimum series noise

- Input MOSFET fully optimized:

$$ENC_{sw,opt} \approx \sqrt{kTC_{det}} \sqrt{\frac{\tau_{el}}{t_m}}$$
$$ENC_{1/f,opt} \approx \sqrt{K_F C_{det}}$$

$\tau_{el}$  = electron transit time  
under the gate  
 $= C_{gs} / g_m$

- Key ingredients for low series ENC:
  - *low*  $C_{det}$
  - *long*  $t_m$
  - *short*  $\tau_{el}$
  - *low*  $K_F$

# Gate resistance noise

- Polysilicon gate is resistive:

- $\rho_{poly}$ 
**25  $\Omega/sq.$**

- $\rho_{silicided\ poly}$ 
**4  $\Omega/sq.$**


resistance of non-interdigitated gate:

$$R_g = \rho_{poly} \cdot \frac{W}{L}$$

series noise due to gate resistance:

$$e_{ng}^2 = 4kT \cdot R_{eq}$$

FET with interdigitated layout

 


n gate fingers  
n = 4

Layout	Req driven one end	Req driven both ends
Single finger	$R_g/3$	$R_g/12$
Interdigitated n fingers	$R_g/3n^2$	$R_g/12n^2$


# Bulk resistance noise

- Resistive substrate couples to the channel via the back transconductance  $g_{mb}$ .
- Substrate resistance is distributed.

*leads to noise in the channel:*

 

 
$$i_{db}^2 = \left[ 4kT \cdot n \cdot \beta \frac{d}{\left(\frac{W}{n}\right)} \cdot \left(\frac{g_{mb}}{n}\right)^2 \right] = 4kT\beta \frac{d}{W} g_{mb}^2$$




- Minimize by reverse biasing the source-substrate junction.

# Layout techniques to reduce gate and bulk resistance noise


Waffle iron layout

 

 Substrate contacts, guard ring, multiple gate fingers contacted on both ends




# Preamp reset – requirements

 

- all charge preamplifiers need DC feedback element to discharge the input node and stabilize the bias point
- usually, a resistor in the  $M\Omega - G\Omega$  range is used
- monolithic processes don't have high value resistors
- we need a circuit that behaves like a high resistor and is also
  - *insensitive to process, temperature, and supply variation*
  - *low capacitance*
  - *lowest possible noise*
  - *linear*

 
# Preamplifier reset – monolithic techniques (1)



$$i_n^2 = \frac{4kT}{\text{Re}\{Z_{in}\}}$$
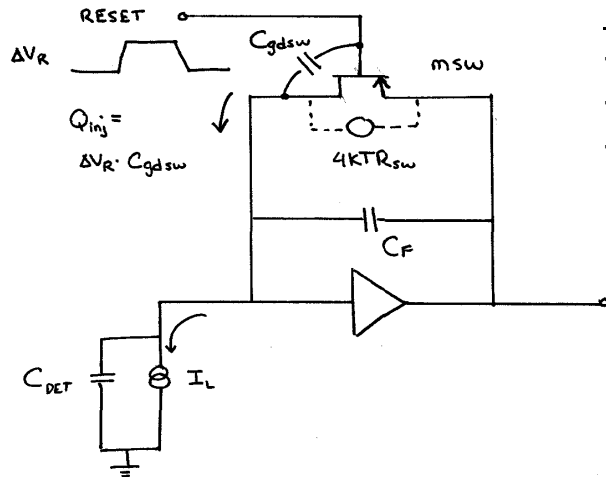
## Physical resistor


- always accompanied by parasitic capacitance
- de-stabilizes circuit and increases noise
- noise higher than  $4kT/R$  by factor  $\sim RC/t_m$



## Pulsed reset by MOS switch


- sampled noise  $\sqrt{kTC_F}$
- $Q_{inj}$  noise from switch control voltage
- leakage current integrates on output node  $dV_{out}/dt = I_L/C_F$
 
# Preamplifier reset – monolithic techniques (2)



O'Connor et al., TNS v44 n3 (1997)  
 De Geronimo et al., NIM A421 (1999)  
 De Geronimo et al., TNS v47 n4 (2000)

 
- provides effective current gain  $-N$
- full compensation (high linearity)
- minimum noise (thermal)
- requires baseline stabilization
- can be realized in multiple stages



Krummenacher, NIM A350 (1991)  
 Ludewigt et al., TNS v41 n4, (1994)  
 Vandebussche et al., TNS v45, n4 (1998)  
 Manfredi et al., Nucl.Phys.B 61B, Proc.Suppl. (1998)


- noise can be high
- requires baseline stabilization at high rates
- compensation an issue
 
# Preamplifier reset – monolithic techniques (3)



Santiard et al., CERN-ECP/94-17 (1994)  
Chase et al., NIM A409 (1998)  
Sampietro et al., Elec.Lett. v34 n19 (1998)

 - noise can be high (large values of R and N required)
- linearity an issue
- parasitic capacitor an issue
- compensation available in some configurations
- requires baseline stabilization




Blanquart et al., NIM A395 (1997)  
Blanquart et al., NIM A439 (2000)

- MOSFET operates in saturation only when there is signal activity
- noise can be high (it requires  $I_{bias} > I_{det}$ )
- parasitic capacitor an issue
- suitable for Time-Over-Threshold processing techniques
- requires baseline stabilization at high rates
- linearity an issue
- compensation an issue




# Nonlinear pole-zero compensation

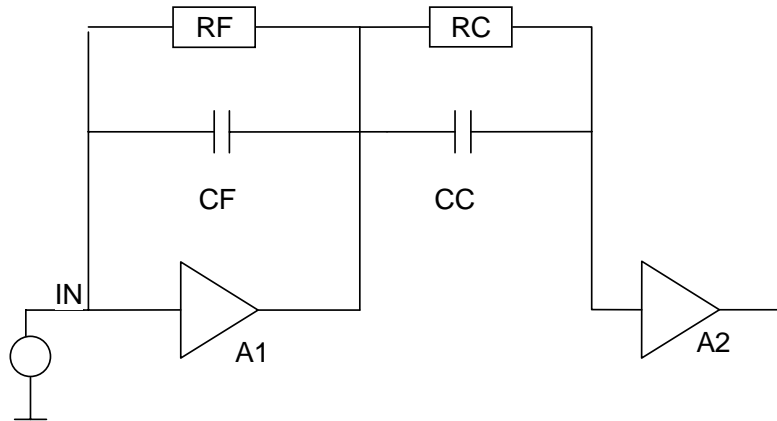

- Classical

 - $RF \cdot CF = RC \cdot CC$
- Zero created by  $RC$ ,  $CC$  cancels pole formed by  $RF$ ,  $CF$




- IC Version

- $CC = N \cdot CF$
- $(W/L)_{MC} = N \cdot (W/L)_{MF}$
- Zero created by  $MC$ ,  $CC$  cancels pole formed by  $MF$ ,  $CF$
- Rely on good matching characteristics of CMOS FETs and capacitors


G. Gramegna, P. O'Connor, P. Rehak, S. Hart, "CMOS preamplifier for low-capacitance detectors", NIM-A 390, May 1997, 241 – 250.

# Preamp reset with nonlinear PZ compensation – experimental results

linearity

 

output vs pixel leakage current

 


# Compensated reset system

---

- Advantages:
  - *near theoretical noise contribution*
  - *accepts detector leakage current over wide range*
    - allows DC coupling of detector to preamp
  - *compensate the parasitic preamp feedback pole with a precisely matched zero*
    - allows crude single-element feedback
  - *insensitive to variations in supply voltage, temperature, and process*
  - *internal bias circuit needs no external adjustments*
    - same circuit works for any detector, gain, tp
  - *easy to implement programmable gain*
- Drawbacks:
  - *only works in one polarity*
  - *DC leakage amplified by same factor as signal*
    - requires BLR in 2<sup>nd</sup> stage
  - *large area consumption*

 
# Secondary noise sources in the preamp

- $i_{B1}^2$  and  $i_{B2}^2$  are effectively in parallel with the input transistor
- Their contribution to input (white) thermal series noise is  $(g_{mB1,2}/g_{m1})^2$ .
- We minimize their  $g_m$  w.r.t. that of M1
- $g_{mB1,2} = \sqrt{2\mu C_{ox} W I_D}/L$
- use low W/L (i.e. long-gate) devices with large or degenerate with source resistor.
- Keep W/L as small as possible (thus  $V_{gs} - V_T$  large) while keeping  $V_{DS} > V_{gs} - V_T$ .
- Various ways to optimize.



# Shaper and baseline stabilizer


---

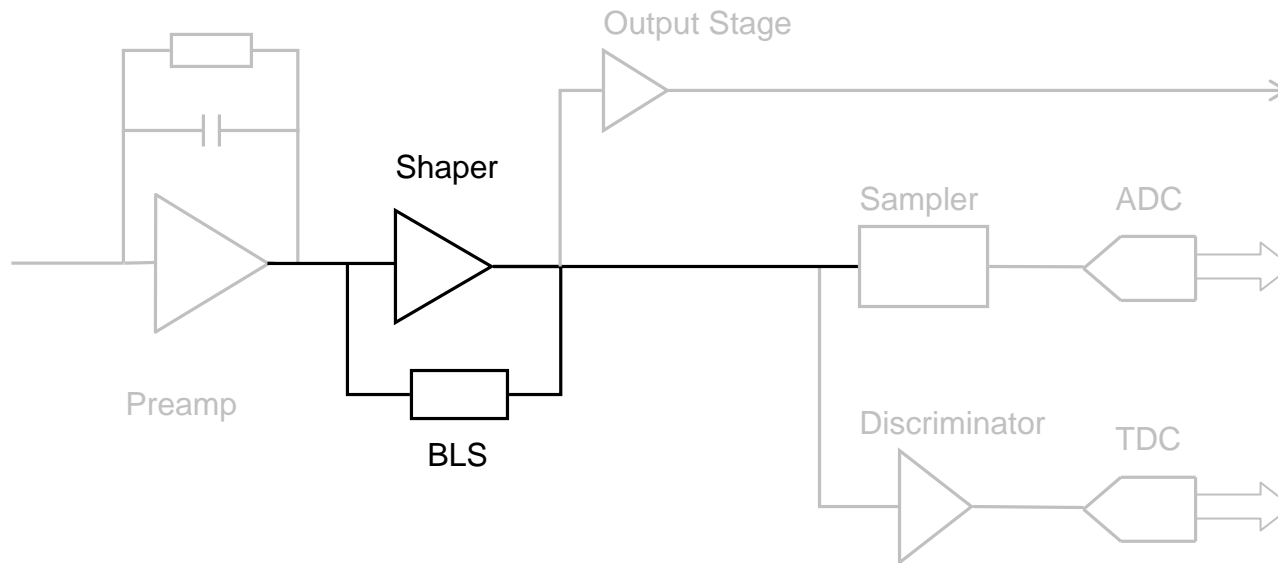

# Integrated shaping amplifiers

- Limits the bandwidth for noise
- Gives controlled pulse shape appropriate for rate
- Control baseline fluctuations
- Set slope at threshold crossing for timing
- Bring charge-to-voltage gain to its final value
- By its saturation characteristics, sets upper limit on  $Q_{in}$
- Feedback circuits give the most stable and precise shaping
  - *At the expense of power dissipation*
  - *Poor tolerance of passives limits accuracy of the poles and zeros*
- High-order shapers give the lowest noise for a given pulse width

## Shaper Characteristics

 

*first and second moments*

$$\int_{-\infty}^{\infty} |h(t)|^2 dt$$

$$\int_{-\infty}^{\infty} |h'(t)|^2 dt$$

*slope at threshold crossing*

$$h'(t_{TC})$$



$$\text{where } h(t_{TC}) = V_{th}$$

# Pulse shaper – matched filter with compromises

- calculation of matched filter
  - *incomplete knowledge of noise spectrum*
  - *incomplete knowledge of input waveform*
- exact transfer function difficult to realize in practice
- optimum filter requires a long time to respond
  - *pileup  $\Leftrightarrow$  limited rate capability*
- “ballistic deficit”
  - *input charge is not a  $\delta$ -function*
  - *width of impulse response must be  $\gg$  duration of input charge waveform*


constraints:

  - noise corner
- rate<sup>-1</sup>
- charge collection
- preamp decay




# Pulse shaping filters with real poles

## Simplest filter: CR-RC

 


- asymmetric response

 
## CR-RC<sup>n</sup>, unipolar semiGaussian



 - Identical real poles
- Symmetry improves with order  $n$ :


 
## CR<sup>2</sup>-RC<sup>n</sup>, bipolar semiGaussian




- Area-balanced
- Derivative of CR-RC<sup>n</sup>



# Properties of real-pole semiGaussian shapers

unipolar CR-RC<sup>n</sup>

 


$$H_u(s) = \frac{s\tau}{(1+s\tau)^{n+1}}$$

$$h_u(t) = \frac{1}{n!} \left( \frac{t}{\tau} \right)^n e^{-t/\tau}$$

$$t_p = n\tau$$

bipolar CR<sup>2</sup>-RC<sup>n</sup>

 

$$H(s) = \frac{(s\tau)^2}{(1+s\tau)^{n+2}} \quad \omega_{\max} = \frac{2}{n\tau}$$

$$h(t) = \frac{1}{(n+1)! \tau} \left( \frac{t}{\tau} \right)^n e^{-t/\tau} [t - (n+1)\tau]$$


$$t_{p1} = (n+1 - \sqrt{n+1})\tau$$

$$t_{zc} = (n+1)\tau$$

$$t_{p2} = (n+1 + \sqrt{n+1})\tau$$

# Complex pole approximation to Gaussian pulse

Shaper Pole Positions

 

Ohkawa synthesis method (Ohkawa, NIM 138 (1976) 85-92, "Direct Syntheses of the Gaussian Filter for Nuclear Pulse Amplifiers")

For given filter order, gives closest approx. to a true Gaussian


More symmetrical than CR-RC<sup>n</sup> filter of same order for same peaking time

Noise weighting functions:



$$I_{1,\text{complex}}/I_{1,\text{CR-RC}} = 1.18 \quad \text{series}$$

$$I_{2,\text{complex}}/I_{2,\text{CR-RC}} = 0.81 \quad \text{parallel}$$


# Shaper optimization

 

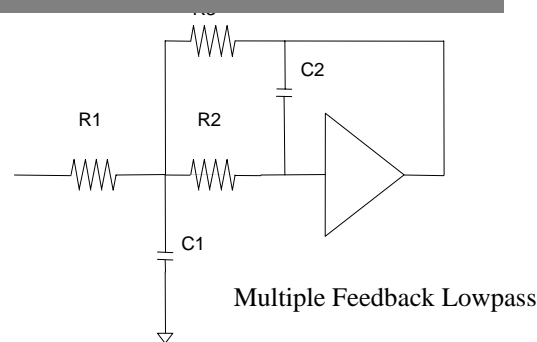 
- For a given rate-handling capability, high-order shapers have lower noise.
- Adding an extra shaper stage can reduce noise more than putting the equivalent amount of power into the preamp.
- For a given shaper order, complex pole constellation using second- or third-order active filter topologies minimizes noise.




Shaper Pole Positions

 

# Second-stage noise

 

Transform  $e_B$  to the input:

 


$$\frac{ENC_B}{ENC_A} = \frac{C_F}{C_D} \cdot \left( \frac{R_B}{R_A} \right)^{1/2}$$

# Baseline stabilization


Baseline can move due to:

1. DC coupling to detector with variable leakage
2. Temperature and power supply drift
3. Rate fluctuations in a system with AC coupling

 
(1) and (2) can be prevented by low frequency feedback circuit:



Result:

 


 **But** this introduces unintended AC coupling:



 
# Area balance after AC coupling

- Unipolar pulse:
- baseline displaced below 0
- instantaneous rate fluctuations cause baseline to wander




 - Bipolar pulse:
- each pulse is area balanced, no detrimental effect of AC coupling
- penalty is higher noise, longer occupancy per pulse




# Output stage

---

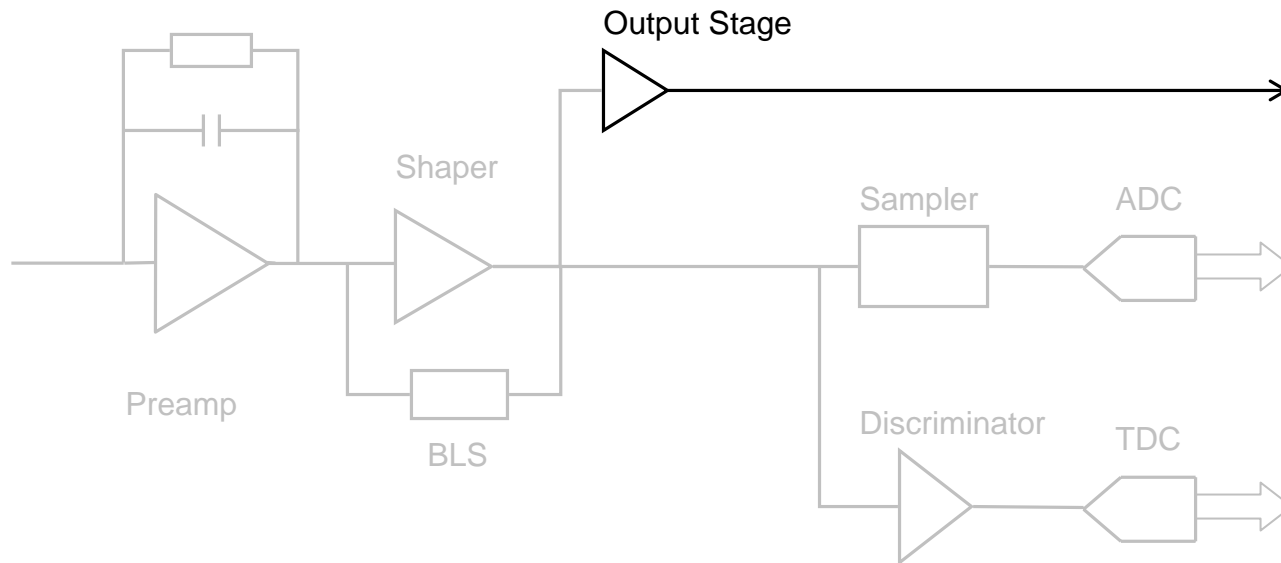


# Output driver

source follower

 

- class A: high standing current
- can't swing rail-to-rail

class AB common source

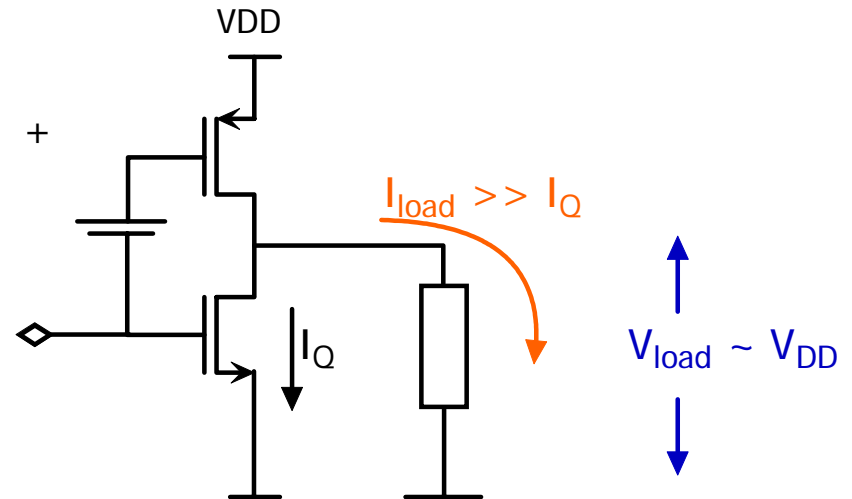


- class AB stage can source or sink currents  $\gg$  quiescent current
- common-source stage can drive rail-to-rail




# Analog sampling

---

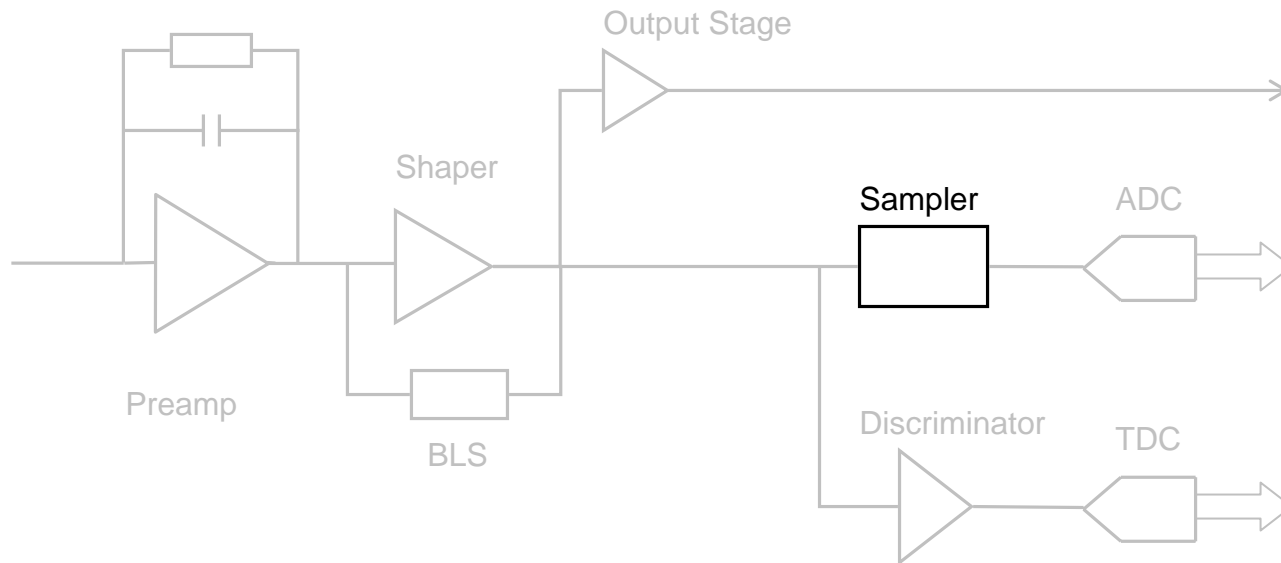


# Candidate sampling/memory cells in CMOS

## Sample/hold using switched capacitor

 

- small
- low-power
- timing of hold signal: needs CFD for walk-free operation
- switch charge injection
- poor drive capability: needs output amp

## Peak Detector (PD)

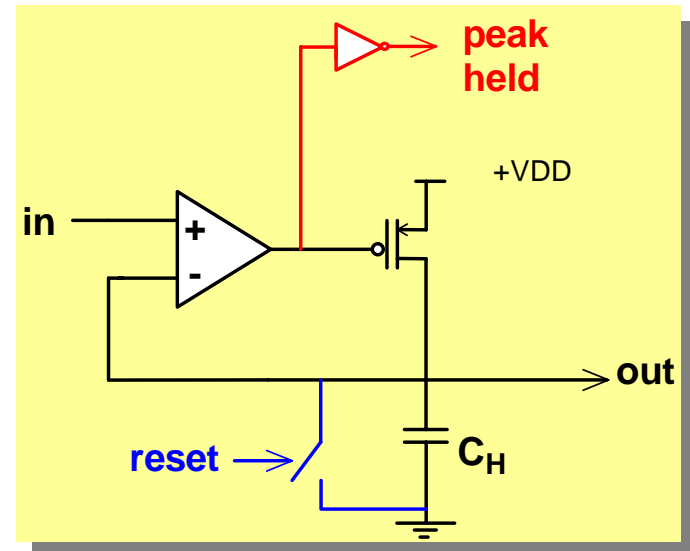

- self-triggered
- timing output
- feedback loop
- deadtime until readout reset
- poor drive capability
- accuracy impaired by opamp offsets, CMRR, slew rate

# Switched-capacitor track-and-hold

TRACK/  
HOLD

$V_{in}$

CMOS  
switch

$C_H$

CMOS switch:



- *low  $I_{off}$*
- *high  $G_{on}$ ,  $0 < V_{sig} < V_{DD}$*

MOS/MIM capacitor:

- *well-matched*
- *low leakage*
- *linear*


Design tradeoffs:

  - *speed – droop rate*
- *speed – charge injection*
- *speed – clock feedthrough*
- *low voltage limits*



# CMOS Peak Detector

Classical peak detector

 



Diode replaced by current mirror acting as rectifying and loop-stabilizing element.

Reduced charge injection from sharp transient at node A(B).

$$\Delta V_A = V_P; \Delta V_B = V_{th} \ll V_P$$

Accuracy, speed, and dynamic range limited.


Improved CMOS version

  

# The two-phase peak detector concept



## Write phase

- behaves like classical configuration

 

  
## Read phase

- op-amp re-used as buffer
- offset** and **CMMR errors canceled**
- enables **rail-to-rail** sensing
- good **drive capability**
- self-switching** (peak found)




P. O'Connor, G. De Geronimo, A. Kandasamy, IEEE Trans. Nucl. Sci. 50(4), 892 (2003)  
G. De Geronimo, P. O'Connor, A. Kandasamy, Nucl. Instr. Meth. A484, 533 (2002)

# Track/hold array + N-to-1 multiplexer

 


- tradeoff of multiplexing ratio, deadtime
- good channel-channel matching
- requires external signal to control track/hold
 
# Switched-capacitor array waveform recorder




# Deadtimeless SCA with simultaneous R/W

 






# Discriminator



---

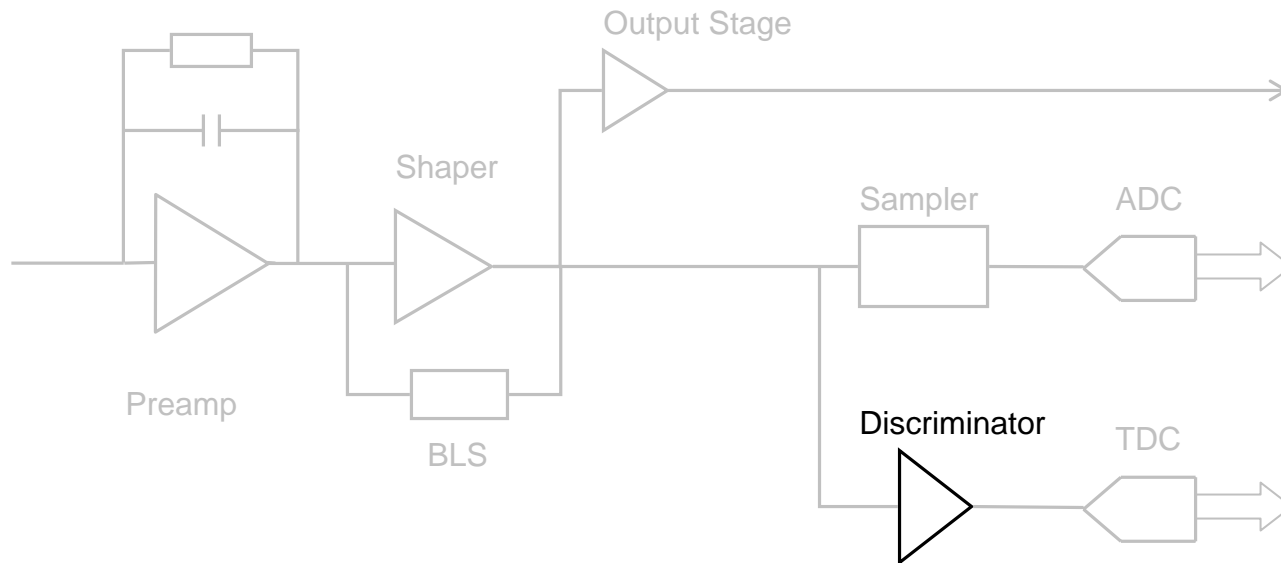
   
# Discriminator properties and applications





  - Characteristics
  - propagation delay*
    - vs. overdrive
    - vs. risetime (of input wfm)
    - vs. load capacitance
  - hysteresis*
  - recovery from saturation*
- Used for
  - hit detection (YES/NO)*
  - trigger*
  - amplitude windowing*
  - amplitude spectra (by threshold sweep)*
  - time interval marker*




Noise hit rate in threshold detection:  
System bandwidth  $B$ , rms noise  $\sigma \rightarrow$
  
$$f_{noise} \approx 0.6B \exp\left(-\frac{V_{th}^2}{2\sigma^2}\right)$$




# CMOS discriminator topologies (1)

 


- Main differential pair M1-M2 plus dual current mirrors provide gain  $\sim 500$
- Cross-coupled pair M1a, M2a provide positive feedback.
- Hysteresis level adjustable by I2/I1 ratio.
- Balanced, fully differential circuit less prone to feedback oscillation.

# CMOS discriminator topologies (2)

 


- Cross-coupled pair M1a, M2a provide positive feedback
- Hysteresis level adjustable by M1/M1a width ratio

# Cascade topology

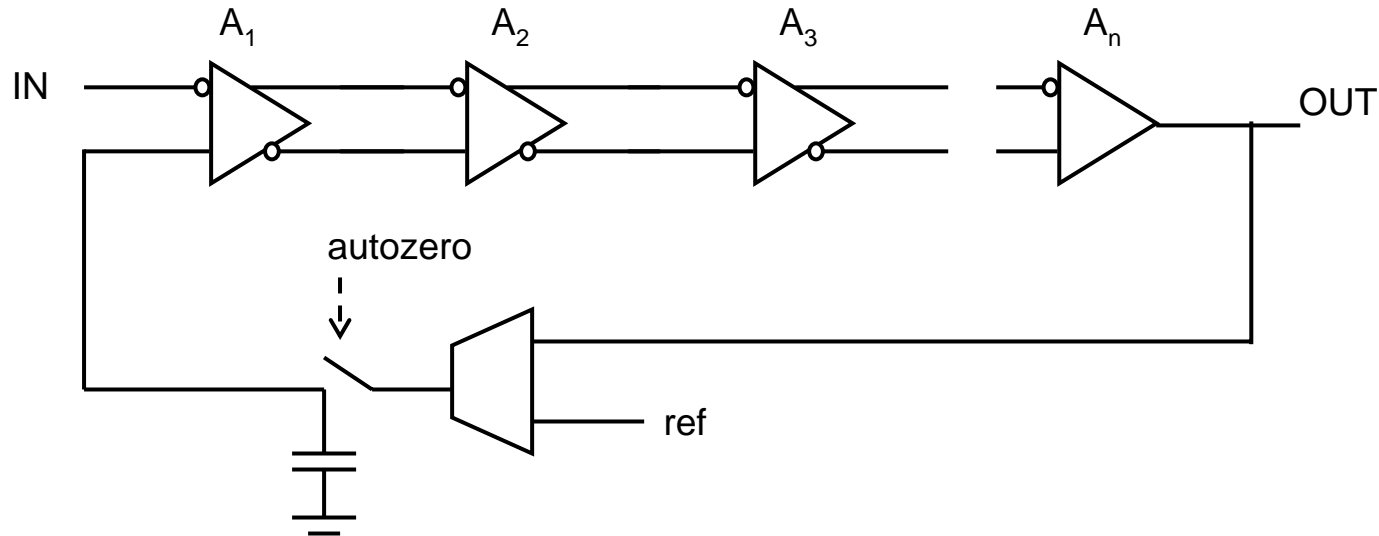

gain stage

 


Overall gain  $A_V^n$


Overall BW  $f_0 \sqrt{2^{1/n} - 1}$

- Cascade gain increases faster than bandwidth decreases as add more stages.
- Nonlinearities limit  $n$  to  $\sim 5 - 6$  in practice.

# Peak detector as timing comparator

 


$C_h$  may be precharged to threshold

 

$V_{out}$  is free of time-walk

# Clocked comparator

 

$\phi=0$ :


M3 holds latches in balanced condition

$\phi=1$ :

M3 OFF, M1/M2 unbalance latches, positive feedback gives rapid response


- This topology frequently used in ADCs.

 Comparator offset cancellation by autozeroing



 
# Non-delay-line constant fraction discriminators



Traditional CFD *delay line not available in CMOS*



 Non-delay-line CFD *filter (lowpass or highpass)*




Simple monolithic implementation

  


$i(t)=0$  when  $dV_C(t)/dt=0$ , i.e. at peak of lowpass waveform  
**independent of amplitude of  $V_{shaper}(t)$**

 Higher-order filter improves slope at zero-cross and leading-edge sensitivity






# Analog-to-digital converter (ADC)

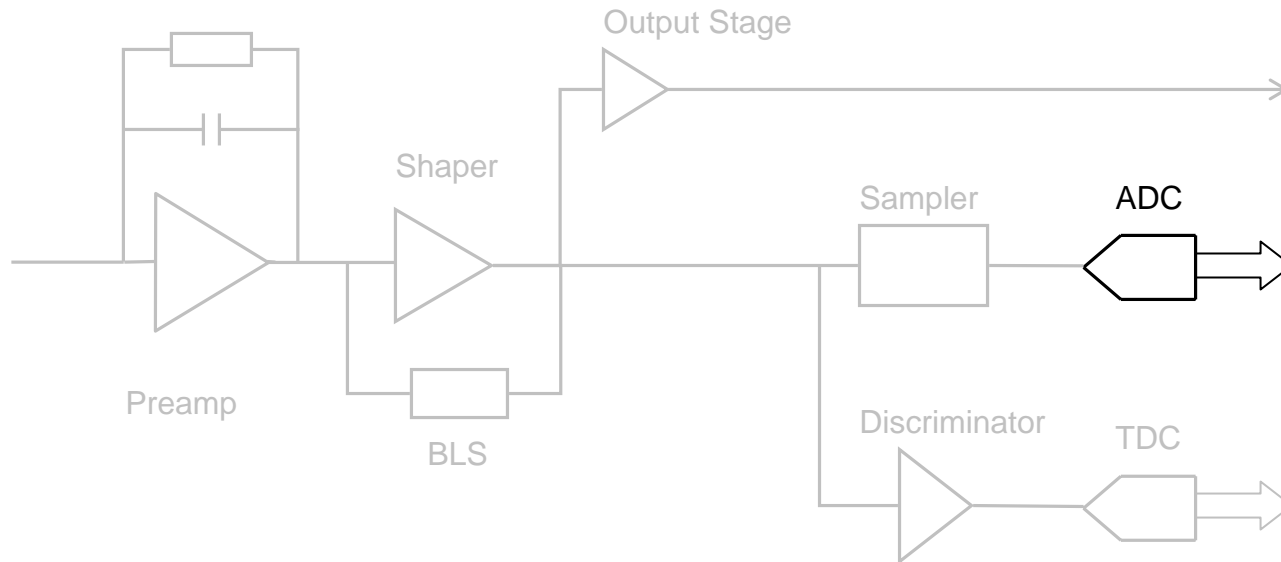


# ADC architectures

 



Tradeoffs:

- speed
- power
- resolution


# Flash converter

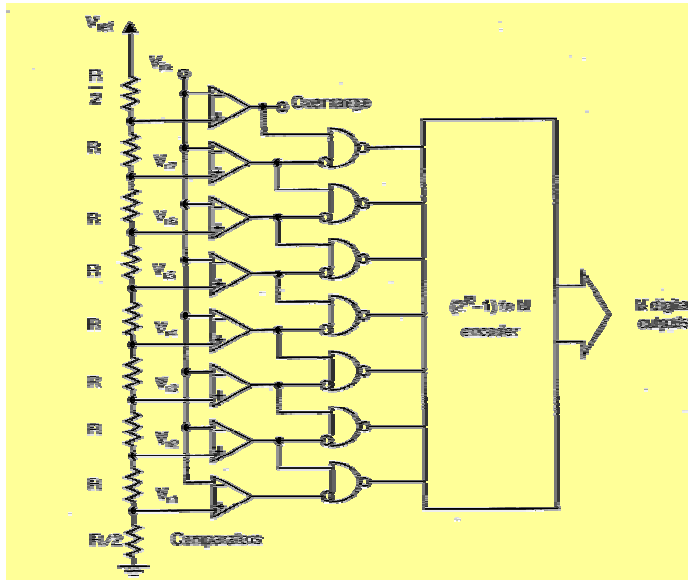

 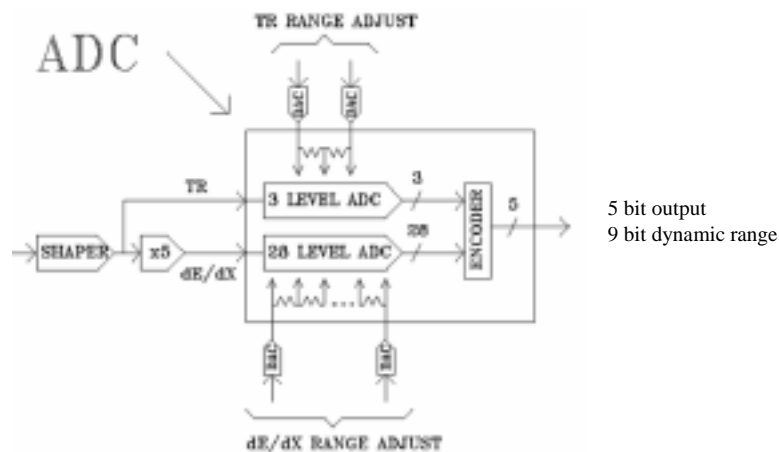- N-bit converter requires  $2^N-1$  comparators and resistors
- Converts in one clock cycle (no latency)
- Comparator offset must be  $< V_{FS}/(2^N)$
- $V_{in}$  must be able to drive large dynamic load of comparator array
- Resistor string may be tapped for piecewise-linear transfer function




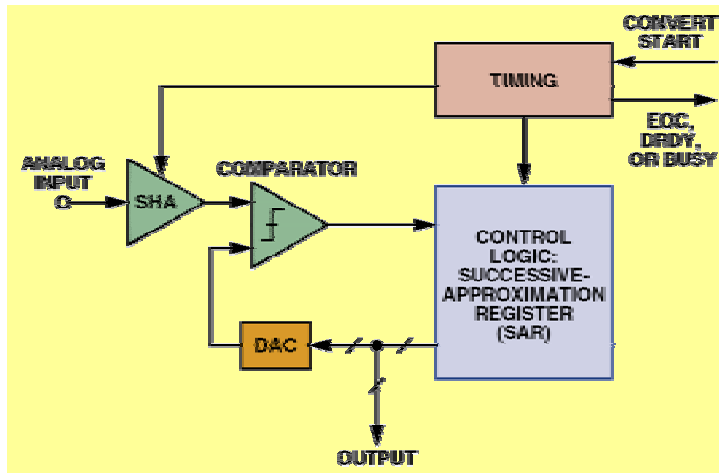
# Successive Approximation (SAR) converter



- Performs binary search using N-bit accurate DAC
- Charge-redistribution DAC gives 10 bit accuracy without calibration for typical 0.1% capacitor matching
- With digital autocalibration accuracy improves to 18-bit
- N-bit conversion requires N comparisons
- Sample-and-hold required at input so value to be converted does not change during the conversion time

  
## Charge Redistribution DAC Example: 4Bit DAC- Input Code 1011




$$Q = V_{ref} (8C + 2C + 1C) = V_{ref} * 11C$$

$$V_{ref} * 11C = V_{out} * 16C$$
 
$$\rightarrow V_{out} = \frac{11}{16} V_{ref}$$




## Binary search

 


In SAR converter, CDAC also combines functions of sample/hold and subtractor

# Single-slope (Wilkinson) integrator

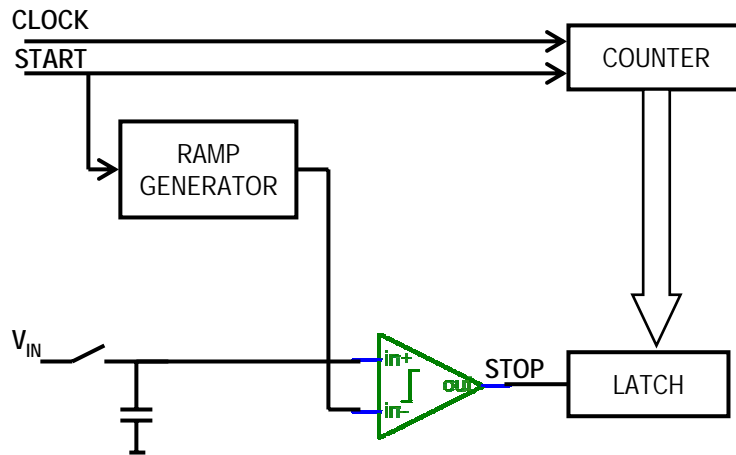



- Converts voltage into time interval
- N-bit conversion requires  $2^N - 1$  clock cycles (worst case)
- Dual-edge clocked, Gray code counter improves speed performance
- Compact, low power
- Easily extended to multichannel systems

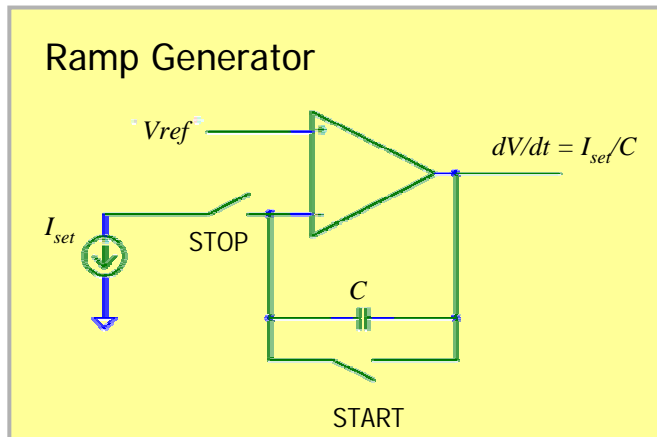- *counter, ramp generator common to all channels*
- *Sample/hold, comparator, and output register per channel*




O. B. Milgrome, et al, "A 12 Bit Analog to Digital Converter for VLSI Applications in Nuclear Science," *IEEE Transactions on Nuclear Science*, Vol. 39, No. 4, pp. 771-5, 1992.

# Dual-slope integrator

 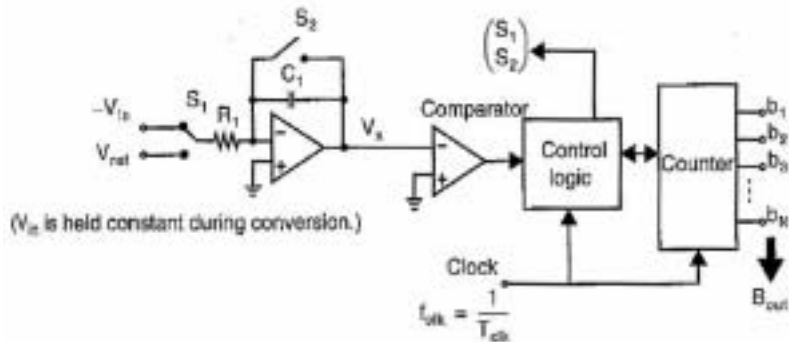


- Compare  $V_{in}$  to reference voltage by measuring time needed to charge/discharge  $C_1$
- $2^N$  clock cycles per conversion, worst case
- Result independent of  $R_1, C_1$ , comparator offset
- Largely supplanted by oversampling  $\Sigma-\Delta$  converters in most commercial markets

# Pipeline converter

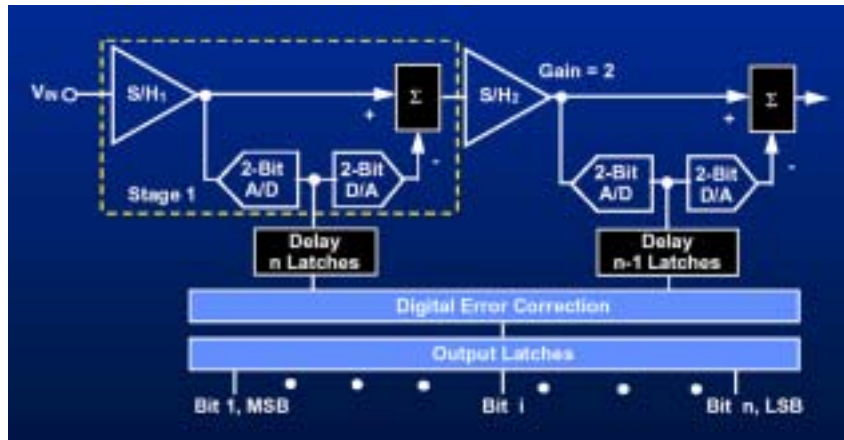





- Cascade of N stages, each stage consists of a sample/hold, low resolution ADC and DAC, summing amplifier with gain-of-2
- Each stage converts one bit and passes the residue on to the next stage
- N samples being simultaneously processed
- High throughput, moderate complexity, low power
- Only first stage needs full accuracy
- Sub-converter nonidealities can be removed by digital error correction
- Latency of N clocks between sample and valid data
- Minimum clock rate because of droop of internal S/H's
- Cannot be operated in burst mode

# Time-to-digital converter (TDC)

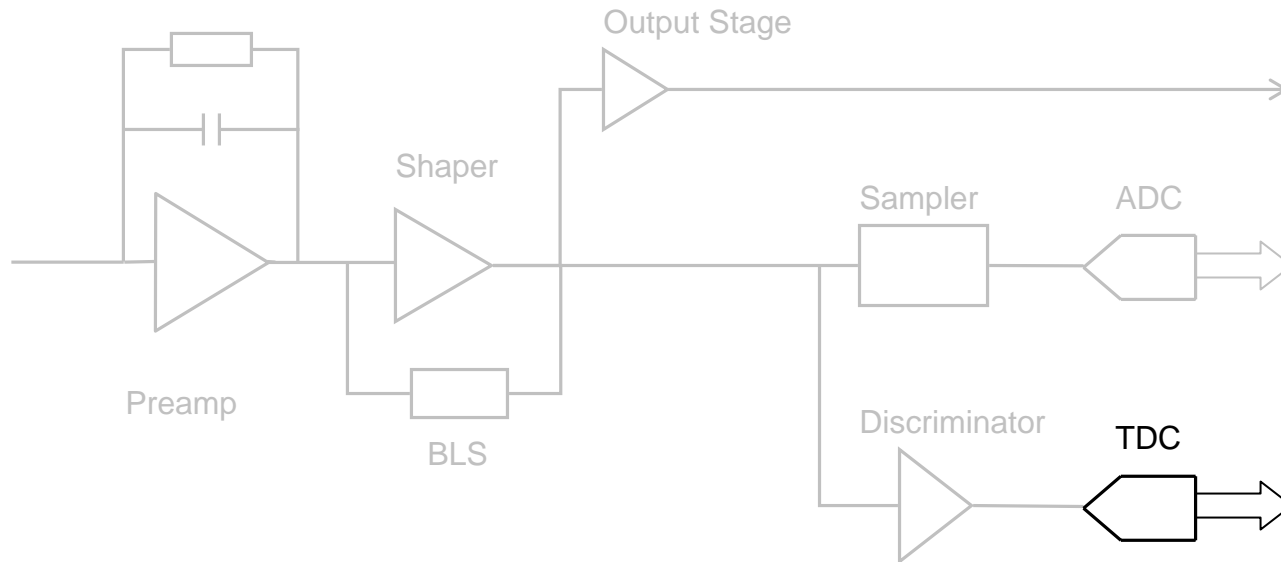




# Time-to-amplitude converter (TAC)

 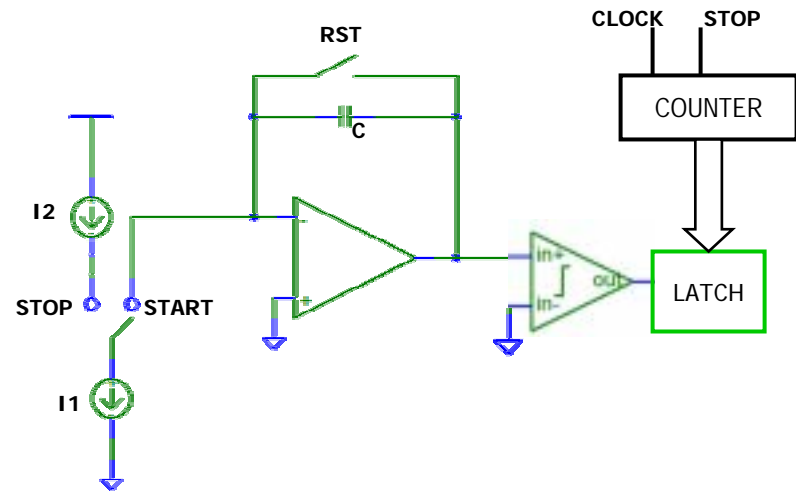 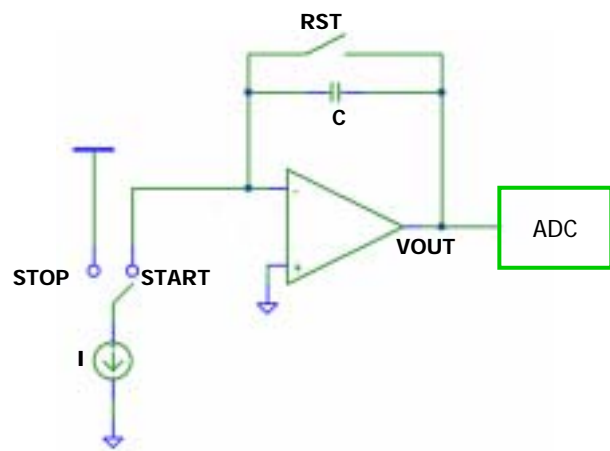



# Delay-locked loop interpolator

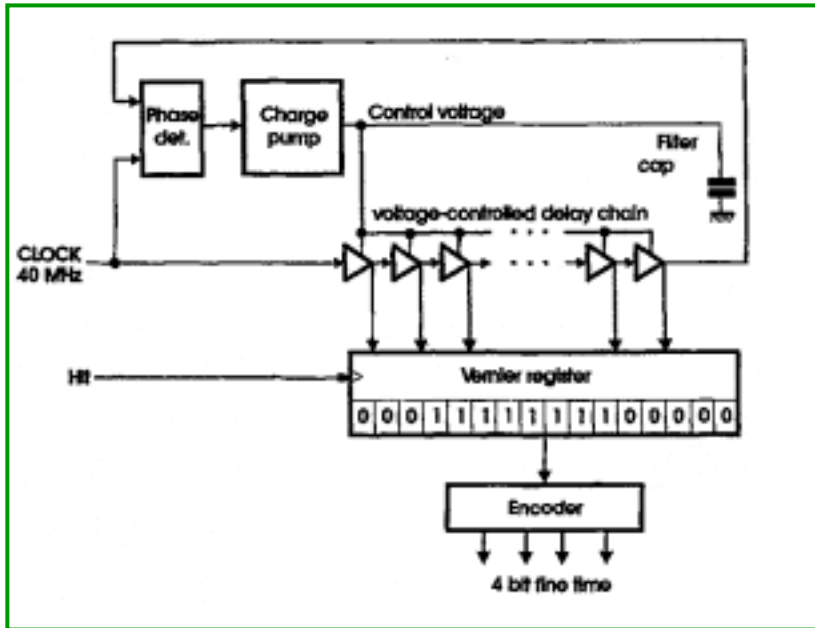


- Clock (START) signal propagated down a tapped, N-element delay chain
- Hit (STOP) freezes state of delay line
- Delay per stage stabilized to  $T_{ck}/N$  by phase-locking output to input, using voltage control of delay elements
- Resolution  $T_{ck}/N$ ; dynamic range  $T_{ck}$
- Extend dynamic range by coarse counter
- Mismatch of delay elements  $\rightarrow$  nonlinearity
- Long delay lines more nonlinear
- Easily extended to multichannel systems:
  - *DLL common to all channels*
  - *Latch, encoder per channel*

Variable delay element

Phase detector

  


# Pulse-shrinking TDC

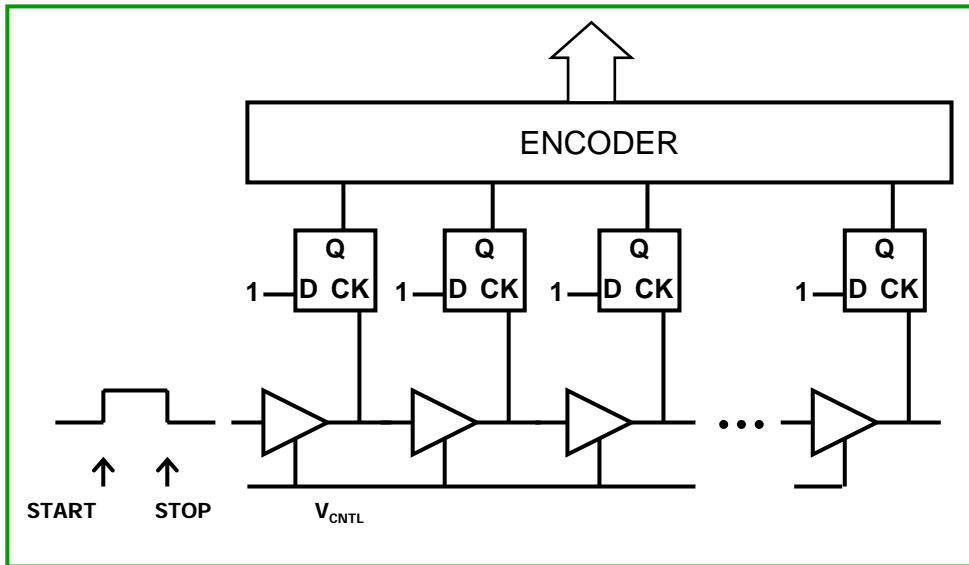


- Chain of pulse-shrinking elements
- Change of pulse width  $\Delta t$  per cell (stabilized)
- After  $n$  cells the pulse width shrinks to zero
- Cyclic version recirculates pulse through same shrinking element; count number of cycles until pulse vanishes
- Resolution LSB can be  $\ll t_{pd}$  of the technology
- Conversion time  $>$  time interval to be measured
- Both schemes can be combined with coarse counters to extend dynamic range

Cyclic version

 

# Vernier DLL principle

 

- START and STOP signals propagate down separate delay lines
- START chain has longer element delay than STOP
- Measure the stage where STOP catches up to START
- Stabilize by controlling *difference*  $t_1 - t_2$  so that  $N(t_1 - t_2) = T_{ck}$
- Resolution LSB can be  $\ll t_{pd}$  of the technology

---

# **Not in signal path, but important**

- Power conditioning and distribution
- Bias circuits
- Electrostatic discharge protection
- Digital configuration switches
- Analog monitor
- DACs
  - *set comparator thresholds*
  - *trim channel-channel variations*
- Calibration pulser

---


# Packaging, Interconnect, and Systems Issues

Paul O'Connor, Brookhaven National Laboratory

IEEE Nuclear Sciences Symposium/Medical Imaging Conference


October 24, 2009

# Cost of interconnect

 



# Pixel density

 

Doubling every 5 months


# **Interconnect issues in monolithic front ends**

- **Detector – Front End**
  - Lowest possible capacitance for low noise
  - Maintain small form factor
  - Ease of assembly
- **Front end – Data Acquisition**
  - Analog processing to reduce the required level of digitization
    - *sampling*
    - *peak detection*
    - *multiplexing*
  - Efficient use of expensive “analog” interconnect
 
# Detector – FE interconnect choices

- **board-to-backplane**

- easy to test, repair
- large boards possible
- connector pins are failure points
- coarse pitch and high capacitance ( $> 1\text{pF}$ )



- **standard SMT package soldered to board (QFP or BGA)**

- easy to test, difficult to repair
- capacitance down to  $0.2\text{ pF}$  for small packages
- board area limited by reflow oven capacity




- **wirebonded chip-on-board**

- difficult to test, assemble, and repair
- board area limited by wirebonder
- fragile
- low capacitance ( $0.1\text{ pF}$ )




- **bump-bonded flip-chip**

 - can match pixels with pitch from  $\sim 30 - 1000\text{ }\mu\text{m}$
- difficult to test, assemble, and repair
- circuitry has to fit in same area as pixel




- **monolithic detector/electronics**

 - interconnect is created as part of the detector fabrication process
- ultra-low capacitance (few fF)




# Power density

 

- On-detector power density is limited by cooling capability.
- Electronics for high-density detector must be extremely low power.




# Packaging density

 
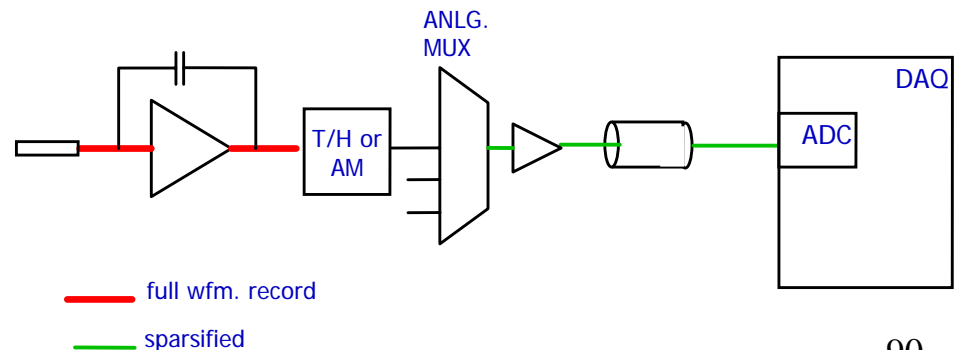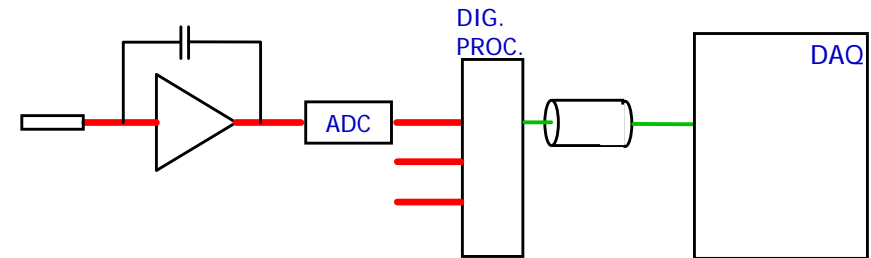 
# Front end – DAQ interconnect

- High bandwidth analog interconnect is expensive and bulky.
- Due to the low occupancy, this interconnect bandwidth is mostly wasted.
- Digitizing every channel is inefficient in a low-occupancy system.
- Existing approaches to sampling and multiplexing are inefficient:


- *track/hold needs trigger, incurs deadtime during readout*
- *analog memory (SCA) deadtimeless but needs trigger, multiple samples, no sparsification, complex controller*





# Putting it all together

---

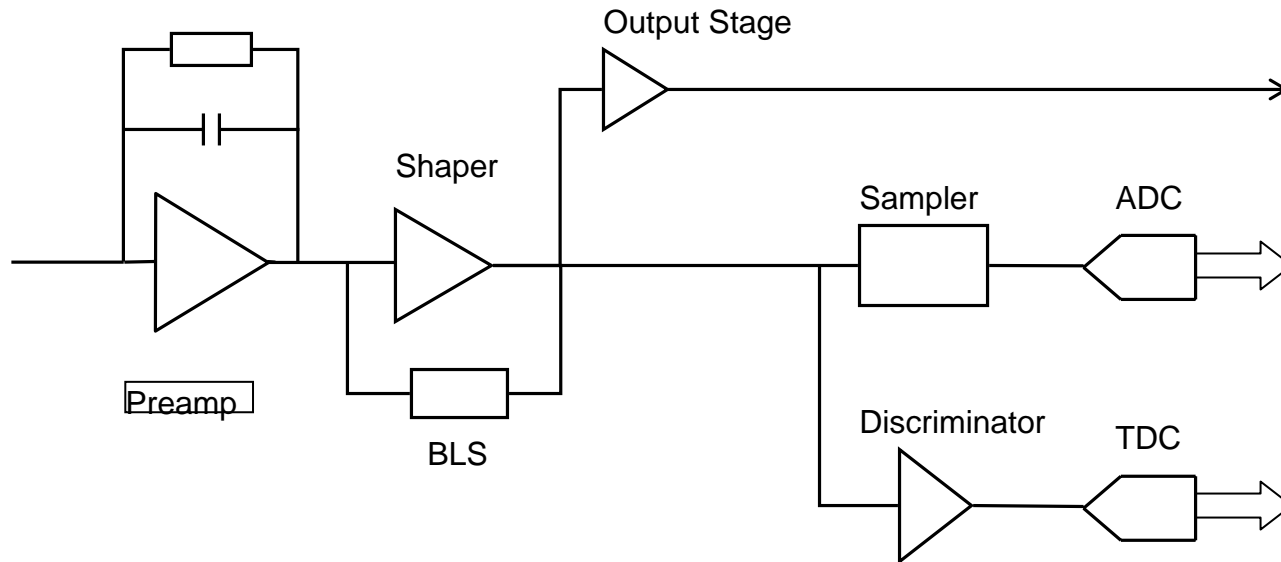



# Power Efficient Architecture

---

- Highest power functions:
  - *charge preamplifier*
  - *analog line driver*
  - *ADC*
- Staying within a power budget and achieving maximum performance involves careful tradeoff.

## Figure of merit for charge amplifiers and ADCs

$$FOM_{CSA} = \frac{P_d \cdot \tau_p}{Q_{\max} / \sigma_Q}$$

- Expresses the power cost of achieving SNR and speed
- Can be applied to front ends in any technology
- Corresponds to figure of merit for analog-digital converters:

$$FOM_{ADC} = \frac{P_d}{2^{ENOB} \cdot f_s}$$

# Rule-of-thumb estimates

- Use  $FOM_{CSA} \sim 1\text{pJ}$ , calculate most quantities of interest.
- Given  $P_{max}$ , rate  $r$ , what is achievable SNR?

$$SNR = \frac{P}{FOM_{CSA} \cdot 10r}$$


– e.g.  $P=1\text{mW}$ ,  $r=100\text{kHz}$ ,  $SNR \sim 10^3$

- What power needed to get timing accuracy  $\sigma_t$ ?

$$\sigma_t \approx \frac{\sigma_V}{dV/dt} \sim \frac{\tau_p}{SNR}; \quad P = \frac{FOM_{CSA}}{\sigma_t}$$

– e.g.  $\sigma_t=2\text{ns}$ ,  $P \sim 50\mu\text{W}$
 
# Figure of merit for charge amplifiers ( $FOM_{CSA}$ ) vs. detector capacitance




Medipix-2

Llopart et al., TNS49(2002)2279

PSI-46

Erdmann et al., NIMA549(2005)153
 
# Figure of merit for ADCs ( $FOM_{ADC}$ ) vs. dynamic range



# Architecture choices

---

- Digital waveform recording of every channel requires ADC to have:
  - *same SNR as charge amplifier*
  - *sampling frequency 2X – 20X higher than analog bandwidth*
- **Guarantees**  $P_{\text{ADC}} \gg P_{\text{CSA}}$
- Better architecture: capture and buffer the analog information on the FEE ASIC, then steer samples to the ADC
- Switched capacitors or peak detectors can serve as the sampling cells
- Use analog buffers (memory) with simultaneous READ/WRITE to avoid deadtime

# Example: TPC Digitization Power

- $N_{\text{pads}}$  8000
- $N_{\text{timeslices}}$  500
- $N_{\text{voxels}}$   $4 \times 10^6$
- $t_{\text{drift}}$   $7 \mu\text{s}$
- $f_{\text{trig}}$  2kHz
- Occupancy 2%
- Digitization Energy (12 bit resolution):
  - $10^{-12} \text{J/bit} * 2^{12} * N_{\text{voxels}} = 16 \text{ mJ}$
- Power (FADC):
  - $16 \text{ mJ} / 7 \mu\text{s} = 2000 \text{ W}$  (250 mW/chan)
- Power (buffer and readout at 2 kHz trigger rate):
  - $16 \text{ mJ} / 500 \mu\text{s} = 30 \text{ W}$  (4 mW/chan)

• Compare with 0.75mW/chan for amplifier + 0.6mW/chan for PD + TAC.

• With sparsified readout of only occupied channels buffered in PD:  $P_{\text{ADC}} \sim 0.6 \text{ W}$  (75  $\mu\text{W/chan}$ ).

# Summary

---

- Modern IC technologies, optimized for digital performance, are challenging for analog design but offer exceptional integration density, speed, and radiation tolerance.
- Noise is limited by available power, detector properties, event rate, and the  $1/f$  properties of the technology.
- In addition to optimizing the first transistor, choice of shaping function is also important in noise optimization.
- High-order shapers improve the power/noise tradeoff, and also improve pileup and charge collection performance.
- An empirical figure of merit for charge amplifiers, analogous to that for ADCs, can be used to guide design choices.
- Reducing the number of analog-to-digital conversions and minimizing off-chip analog signal transmission (where possible) improves noise by allowing power to be allocated to the front end.